



United International University (UIU)
Dept. of Computer Science & Engineering (CSE)
Final Exam, Trimester: Summer 2024

Course Code: CSE 113/EEE 2113; **Course Title:** Electrical Circuits

Total Marks: 50; **Duration:** 2 hours

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

Question 1: Answer all the questions.

(12 Marks)

Your friend just built a circuit and connected a 300Ω bulb between a-b points as shown in **Figure 1**. Answer the following questions: [6+2+2+2]

- i) Determine the Thevenin equivalent circuit for the following circuit your friend has built. CO3
- ii) Determine the power absorbed by this bulb. Is the power the maximum power that can be achieved for this circuit? If not, then what should you do?
- iii) Now, your friend connected another bulb with a different resistance instead of the 300Ω bulb and got the same absorbed power. Determine the new resistance of this bulb.

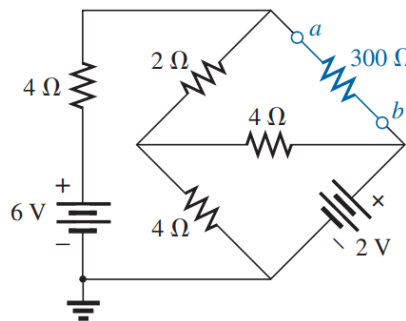


Figure 1

Question 2: Answer all the questions.

(13 Marks)

Determine the value of V_o using the Superposition theorem for the circuit shown in **Figure 2**. Additionally, find the power delivered by the $10V$ voltage source. [10+3]

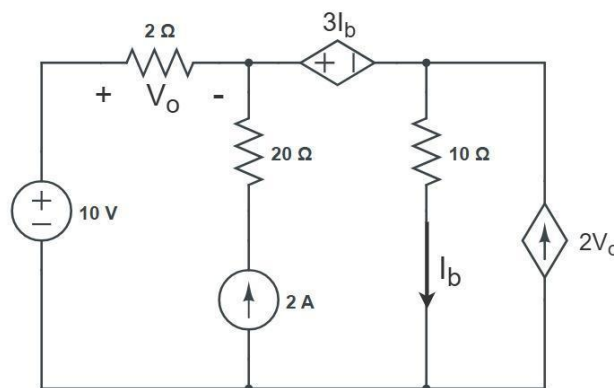


Figure 2

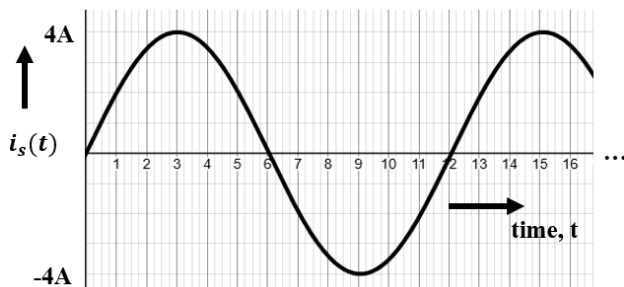
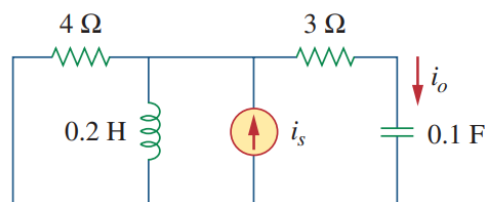
CO3

Question 3: Answer all the questions**(12 Marks)**

An AC current source, $i_s(t)$ [Figure 3(a)] is used in the following circuit shown in Figure 3(b). Answer the following questions:

[2+5+5]
CO4

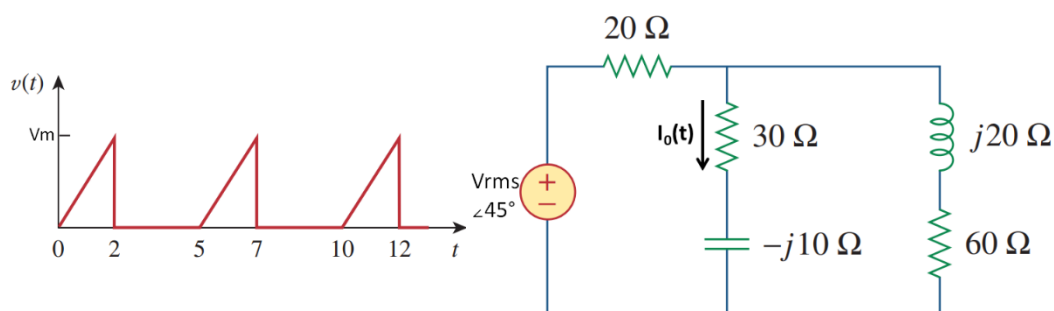
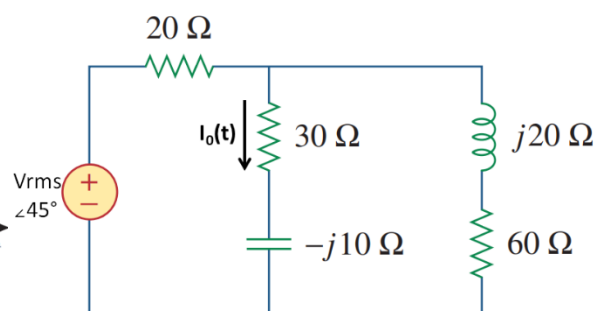
- Determine the equation of $i_s(t)$.
- Determine the equivalent impedance of this circuit.
- Determine $i_o(t)$ and also by how many degrees is $i_o(t)$, leading $i_s(t)$?

**Figure 3(a)****Figure 3(b)****Question 4: Answer all the questions.****(13 Marks)**

When the voltage waveform of Figure 4(a) is applied across a 2- Ω resistor, the average power absorbed by the resistor is 4.267 W. Another AC circuit is shown in Figure 4(b). Now answer the following questions:

[3+5+5]
CO4

- Find the rms value, v_{rms} of the voltage waveform shown in Figure 4(a).
- Find the peak value of the voltage waveform, V_m .
- Use this rms [from (i)] value as the maximum amplitude of the sinusoidal voltage source in the circuit shown in Figure 4(b). Determine $I_o(t)$, and average power absorbed by the 30 Ω resistor in the circuit.

**Figure 4(a)****Figure 4(b)**