

Answer the following questions for the circuit shown in Figure 1:  
 (i) Draw the circuit with the Independent Current Source Turned Off. ii) Draw the circuit with the Independent Voltage Source Turned Off. iii) Apply the Superposition Theorem, and find the value of  $I_R$ .


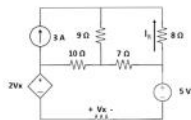


Figure 1.

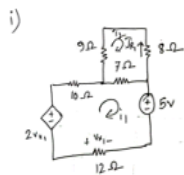

For mesh-1,  
 $5 + 12i_1 - 2V_{s1} + 10i_1 + 7(i_1 - i_2) = 0$   
 $\Rightarrow 5 + 12i_1 - 2(-12i_1) + 10i_1 + 7i_1 - 7i_2 = 0$   
 $\therefore 53i_1 - 7i_2 = -5 \dots (1)$

For mesh-2,  
 $9i_2 + 8i_2 + 7(i_2 - i_1) = 0$   
 $\Rightarrow -7i_1 + 24i_2 = 0 \dots (2)$


Solving (1) and (2) we get,

$$i_1 = -0.098A$$

$$i_2 = -0.0286A$$

$$I_{R1} = -i_2$$

$$= 0.0286A$$

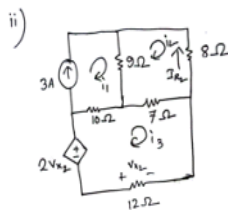

From mesh-1,  
 $i_1 = 3$

For mesh-2,  
 $8i_2 + 7(i_2 - i_3) + 9(i_2 - 3) = 0$   
 $\Rightarrow 24i_2 - 7i_3 = 27 \dots (1)$

For mesh-3,  
 $10(i_3 - 3) + 7(i_3 - i_2) + 12i_3 - 2V_{s3} = 0$

$$\Rightarrow 10i_3 - 30 + 7i_3 - 7i_2 + 12i_3 - 2(-12i_3) = 0 \therefore V_{s3} = -12i_3$$

$$\Rightarrow -7i_2 + 53i_3 = 30 \dots (2)$$

$$i_2 = 1.3418A$$

$$i_3 = 0.7433A$$

$$I_{R2} = -i_2 = -1.3418A$$

iii)  $I_R = I_{R1} + I_{R2}$   
 $= 0.0286 - 1.3418$

$$\therefore I_R = -1.3132A$$

Question 2: Answer all the questions.

(10 Marks)

For the circuit shown in Figure 2, answer the following questions:

- Determine the Thevenin equivalent circuit at the A-B terminal.
- For any value of  $R_L$ , what will be the maximum power delivered to this resistance?
- If  $R_L = 1 \text{ k}\Omega$ , then would maximum power be achieved? If not, then what should you do to achieve maximum power?



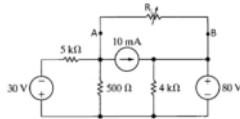


Figure 2.

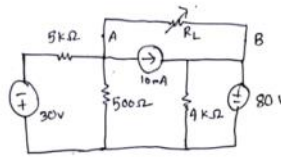


For  $R_{TH}$ ,

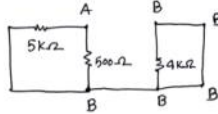

So,  $5 \text{ k}\Omega$  and  $500 \Omega$  are in parallel.

$$\therefore R_{TH} = \left( \frac{1}{5000} + \frac{1}{500} \right)^{-1}$$

$$\therefore R_{TH} = 454.545 \Omega$$

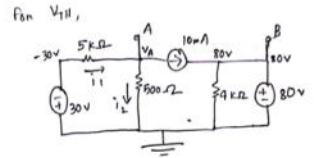

At  $V_A$  node,

$$i_1 = i_2 + 10 \text{ mA}$$

$$\Rightarrow \frac{-30 - V_A}{5000} = \frac{V_A}{500} + 10 \times 10^{-3}$$

$$\Rightarrow -30 - V_A = 10 V_A + 50$$

$$\Rightarrow V_A = \frac{-80}{11} \text{ V}$$

$$V_{TH} = V_A - V_B = \frac{-80}{11} - 80 = -87.2727 \text{ V}$$

ii) Max power

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{(-87.2727)^2}{4 \times 454.545} = 4.18 \text{ W}$$

iii)  $P_{max}$  will not occur for  $R_L = 1 \text{ k}\Omega$

Question 3: Answer all the questions

(10 Marks)

Answer the following questions for the circuit shown in Figure 3:

- i) Determine  $Z_T$ . ii) Current,  $I$ . iii) Find the currents through  $4\Omega$  and  $3\Omega$  resistors.  
iv) Is the source voltage or the current,  $I$  leading in this circuit?

[3+2

+3+2

]

Page 1 of 2


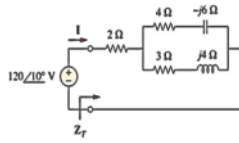


Figure 3.

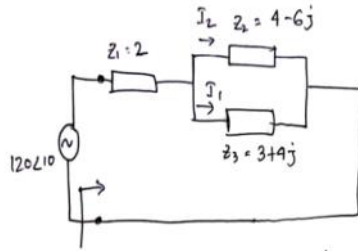

$$Z_T = Z_1 + (Z_2 || Z_3)$$

$$= 6.8302 + 1.0943j$$

$$i) \therefore Z_T = 6.917 \angle 9.103$$

$$ii) I = \frac{V}{Z_T} = \frac{120 \angle 10}{6.917 \angle 9.103} = 17.3478 \angle 0.8974$$

$$iii) I_1 = \frac{Z_2}{Z_2 + Z_3} \times I = 17.183 \angle -39.467^\circ$$

$$I_2 = \frac{Z_3}{Z_2 + Z_3} \times I = 11.9145 \angle 69.9725$$

Current through  $4\Omega$  is  $I_2$   
" "  $3\Omega$  "  $I_1$ .

$$iv) V = 120 \angle 10^\circ = 120 \cos(\omega t + 10^\circ)$$

$$I = 17.3478 \angle 0.8974$$

$$= 17.3478 \cos(\omega t + 0.8974)$$

So,  $V$  is leading.

Question 4: Answer all the questions.

(10 Marks)

For the circuit shown in Figure 4a, determine  $i_m$  if the rms value of such current is 5A. Now, determine  $i_o$  and average real power absorbed by a 3-ohm resistor using CDR in the circuit shown in Figure 4b if the angular frequency is 100 rad/s in the circuit.

[6+2+2]

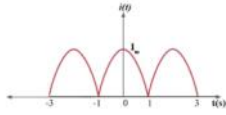


Figure 4a.

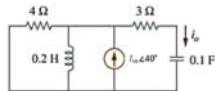


Figure 4b.

Q4: waveform

$$-1 \leq t \leq 1, I_m \cos(\pi t)$$

$$T = 2$$

$$f = 0.5$$

$$\omega = 2\pi f = \pi$$

$$RMS = \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt}$$

$$5 = \sqrt{\frac{1}{2} \int_{-1}^1 I_m^2 \cos^2(\pi t) dt}$$

$$50 = I_m^2 \times 1$$

$$I_m = 5\sqrt{2}$$


$$\frac{1}{2} \int_{-1}^1 1 + \cos 2\pi t$$

$$\frac{1}{2} [1 - \cos 2\pi t] + \left[ \frac{\sin 2\pi t}{2\pi} \right]_{-1}^1$$

$$= 1$$

AC ckt

$$\omega = 100$$

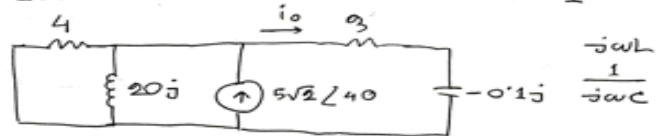

$$(4 + 20j) = 3.84 + 0.777j$$

$$i_o = \frac{3.84 + 0.777j}{3.84 + 0.777j + 3 - 0.1j} \times 5\sqrt{2} \angle 40^\circ$$

$$i_o = 4.03 \angle 45.744^\circ$$

Considering  $I_m$  as peak value

$$Real P_{avg} = \frac{1}{2} |I|^2 R = \frac{1}{2} \times (4.03)^2 \times 3 = 24.36 W$$