

Question 1: Answer all the questions.

(10 Marks)

Use the superposition theorem to determine the value of V_x for the circuit shown in Figure 1. Also, the 8-ohm resistor absorbs power from both independent sources. Analyze the circuit and determine which independent source in this circuit supplies most of the power to the 8-ohm resistor.


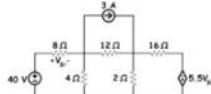


Figure 1

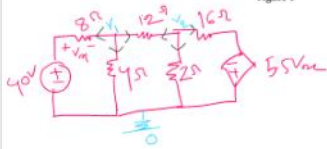

Node V_1 ;

$$\frac{V_1 - 0}{8} + \frac{V_1 - 0}{4} + \frac{V_1 - V_2}{12} = 0$$

$$\Rightarrow \frac{3V_1 - 120 + 6V_1 + 2V_1 - 2V_2}{24} = 0$$

$$\Rightarrow 11V_1 - 2V_2 - 120 = 0 \dots (i)$$

Node V_2 ;

$$\frac{V_2 - V_1}{12} + \frac{V_2 - 0}{2} + \frac{(V_2 - 0) + 5.5V_1}{16} = 0$$

$$\Rightarrow \frac{4V_2 - 4V_1 + 24V_2 + 3V_2 + 16.5V_1}{48} = 0$$

$$\Rightarrow 31V_2 - 4V_1 + 16.5V_1 = 0$$

Hence, $V_1 = V_1 - 40$;

$$\Rightarrow 31V_2 - 4V_1 + 16.5(V_1 - 40) = 0$$

$$\Rightarrow 31V_2 - 4V_1 + 16.5V_1 - 660 = 0 \dots (ii)$$

$$\Rightarrow 12.5V_1 + 31V_2 = 660$$


Solving (i) & (ii);

$$V_1 = 13.77 \text{ V} \quad V_2 = 15.73 \text{ V}$$

$$V_x = V_1 - 40$$

$$= (13.77 - 40) \text{ V}$$

$$= -26.23 \text{ V}$$

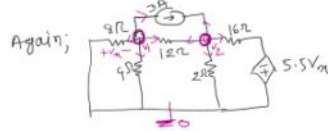

node -1;

$$\frac{V_1}{8} + \frac{V_1}{4} + \frac{V_1 - V_2}{12} + 3 = 0$$

$$\Rightarrow \frac{3V_1 + 6V_1 + 2V_1 - 2V_2 + 72}{24} = 0$$

$$\Rightarrow 11V_1 - 2V_2 + 72 = 0 \dots (i)$$

node -2;

$$\frac{V_2 - V_1}{12} + \frac{V_2}{2} + \frac{(V_2 - 0) + 5.5V_1}{16} - 3 = 0$$

$$\Rightarrow \frac{4V_2 - 4V_1 + 24V_2 + 3V_2 + 16.5V_1 - 192}{48} = 0$$

$$\Rightarrow 31V_2 - 4V_1 + 16.5V_1 = 192$$

here; $V_1 = V_1$

$$31V_2 - 4V_1 + 16.5V_1 = 192$$

$$\Rightarrow 12.5V_1 + 31V_2 = 192 \dots (ii)$$

solving; (i) & (ii); $V_1 = -5.31 \text{ V} \quad V_2 = 6.78 \text{ V}$

$$V_x = V_1 \therefore V_x = -5.31$$

$$V_x = V_x' + V_x''$$

$$= (-26.23 - 5.31) \text{ V}$$

$$= -31.54 \text{ V. Ans.}$$

Power absorbed;

- in 8 Ohm;

$$P = \frac{(V_x)^2}{R}$$

$$= \frac{(-31.54 \text{ V})^2}{8}$$

$$= \frac{994.77}{8}$$

$$= 124.34 \text{ Watt.}$$

Question 2. Answer all the questions. (10 Marks)

For the circuit shown in Figure 2, answer the following questions:
 i) Determine the Thevenin equivalent circuit at the a-b terminal.
 ii) Suppose your friend suggests that if you connect a 20V-40W bulb across a-b terminal, then you will get maximum bulb intensity. Is he right? If not, then calculate the resistance of the bulb that would get maximum intensity.
 iii) Determine the maximum power delivered to the bulb that would be connected across the a-b terminal.


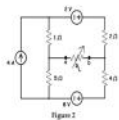


Figure 2

→ simplifying

super mesh

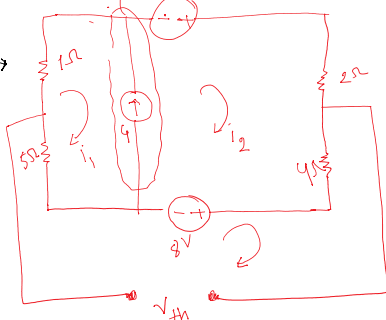

KVL onto Supermesh;

$$6i_1 - 2 + 6i_2 + 8 = 0$$

$$6i_1 + 6i_2 - 6 = 0$$

$$i_1 + i_2 = 1 \quad \text{--- (i)}$$

eqn of supermesh;

$$i_1 + 4 = i_2$$

$$\Rightarrow i_1 - i_2 = -4 \quad \text{--- (ii)}$$

Solving (i) (ii),

$$i_1 = -1.5 \quad i_2 = 2.5$$

KVL onto V_{th} ;


$$\Rightarrow 5i_1 - 8 + 4i_2 + V_{th} = 0$$

$$\Rightarrow 5(-1.5) - 8 + 4(2.5) + V_{th} = 0$$

$$\Rightarrow -7.5 - 8 + 10 + V_{th} = 0$$

$$\Rightarrow -15.5 + 10 + V_{th} = 0$$

$$\Rightarrow V_{th} = 5.5V$$

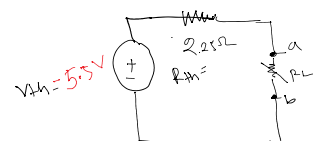

(ii)

We, know, $R_L = R_{th}$

20V-40W; in a-b terminal;

$$P = \frac{V^2}{R}$$

$$\Rightarrow R = \frac{V^2}{P} = \frac{(20)^2}{40} = 10$$

So, $10 \neq 2.25\Omega$

so, my friend is not correct;

$$(iii) P_{max} = \frac{(V_{th})^2}{4R_{th}} = \frac{(5.5)^2}{4 \times 2.25}$$

$$= \frac{30.25}{9} = 3.36 \text{ watt.}$$


Question 3: Answer all the questions

(10 Marks)

For the circuit shown in Figure 3, where $v_g(t) = 247.49 \cos(1000t + \pi/4)$

- Determine the total impedance of the circuit.
- Determine the current through the 100Ω resistor using the current division rule.
- Determine the voltage $V_{ab}(t)$ using VDR.
- Determine by how much degree the voltage $V_{ab}(t)$ is leading the source voltage $v_g(t)$.


[3x3= 2x2] CO4

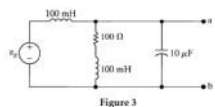

$$v_g(t) = 247.49 \cos(1000t + \pi/4)$$

$$= 247.49 \cos(1000t + 45^\circ)$$

(i) $Z_{eq} = ?$

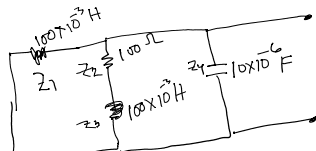

$$Z_1 = j\omega L = j \times 1000 \times 100 \times 10^{-3}$$



$$= 100j \Omega$$

$$Z_2 = 100 \Omega$$

$$Z_3 = 100j \Omega$$

$$Z_4 = \frac{1}{j\omega C} = -j \left(\frac{1}{1000 \times 10 \times 10^{-6}} \right) \Omega$$

$$= -100j \Omega$$

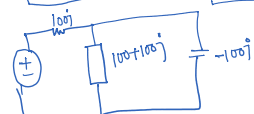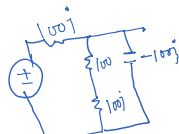

$$Z_{eq} = 100j + 100 - 100j$$

$$= 100 \Omega$$

$$I = \frac{V}{Z_{eq}}$$

$$= \frac{247.49 \angle 45^\circ}{100}$$

$$= 1.75 + 1.75j$$

Current through,

100Ω ;

$$CDR: i = \left(\frac{-100j}{100 + 100j - 100j} \right) (1.75 + 1.75j)$$

$$= 1.75 - 1.75j$$

$$\Rightarrow 2.47 \angle -45^\circ A$$

$$Z_2 = (100 + 100j) \parallel (-100j)$$

$$= \frac{(100 + 100j) \times (-100j)}{(100 + 100j) - 100j}$$

$$= 100 - 100j$$

$$V_g = 247.49 \angle 45^\circ$$

$$VDR: V_{ab} = \left(\frac{Z_2}{Z_2 + Z_1} \right) V_g$$

$$= \left(\frac{100 - 100j}{100 - 100j + 100j} \right) 247.49 \angle 45^\circ$$

$$= 350 V. \Rightarrow 350 \angle 0^\circ$$

(iv)

$$V_{ab}(t) = 350 \cos(1000t + 0^\circ)$$

$$V_g(t) = 247.49 \cos(1000t + 45^\circ)$$

V_g is leading on V_{ab} ; 45° .

Answer the following questions for the circuit shown in Figure 4a:

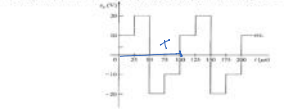


Figure 4a

ii) Now, use this rms value as the maximum amplitude of the sinusoidal voltage source in the circuit shown in Figure 4b. Determine $I_o(t)$ and average real power absorbed by the 2-ohm resistor in the circuit. The angular frequency is 100 rad/s in the circuit.

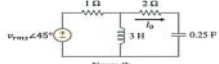


Figure 4b

Here, $T = 100$.

$$(i) \gamma_{\alpha} = \begin{cases} 10 & 0 \angle 25 \\ 20 & 25 \angle 50 \\ -20 & 50 \angle 75 \\ -10 & 75 \angle 100 \end{cases}$$

$$V_{rms} = \frac{1}{T} \int_0^T V^2 dt$$

$$= \frac{1}{100} \left[\int_0^{25} 100 dt + \int_{25}^{50} 400 dt + \int_{50}^{75} 400 dt + \int_{75}^{100} 100 dt \right]$$

$$V_{rms}^2 = 250$$



$$V_{rms} = \sqrt{250} = 15.81 V$$

$$\frac{1}{100} \left(100 \int_0^{25} 1 dt + 400 \int_{25}^{50} 1 dt + 400 \int_{50}^{75} 1 dt + 100 \int_{75}^{100} 1 dt \right)$$

$$= \frac{1}{100} \left(100 \times 25 + 400 \times 25 + 400 \times 25 + 100 \times 25 \right)$$

$$= \frac{1}{100} \left(2500 + 10000 + 10000 + 2500 \right)$$

$$= \frac{25000}{100}$$

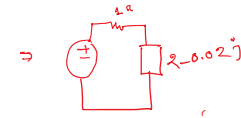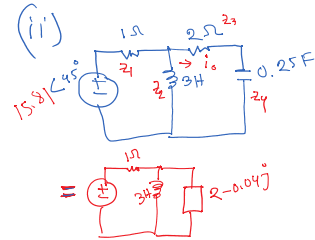

$$Z_{eq} = 2 + 2 - 0.02j = 3 - 0.02j$$

$$I = \frac{V}{Z_{eq}} \Rightarrow \frac{15.81 \angle 45^\circ}{3 - 0.02j} \Rightarrow 3.70 + 3.75j$$

$$Z_1 \parallel (Z_3 + Z_4)$$

$$= \frac{300j \times (2 - 0.04j)}{300j + 2 - 0.04j}$$

$$= 2 - 0.02j$$

$$I_o = \frac{3H}{(2 - 0.04j)} \times 3.70 + 3.75j$$

$$= \frac{300j}{(2 - 0.04j)} \times 3.70 + 3.75j$$

Answer: real power

$$P = \frac{1}{2} |I_o|^2 \cdot R$$

$$= \frac{1}{2} (-573.37) \times 2$$

$$= 328753.1569 \text{ watt}$$

$$I_o = -573.37 + 543.53j$$

Ans: