



UNITED INTERNATIONAL UNIVERSITY (UIU)

Dept. of Computer Science & Engineering

Trimester: Fall 2024 (Assignment 1)


Course No: EEE 2113 Course Title: Electrical circuits

Marks: 50


Problems to solve:

1. The voltage and current at the terminals of a circuit element are shown in Fig below. [10]

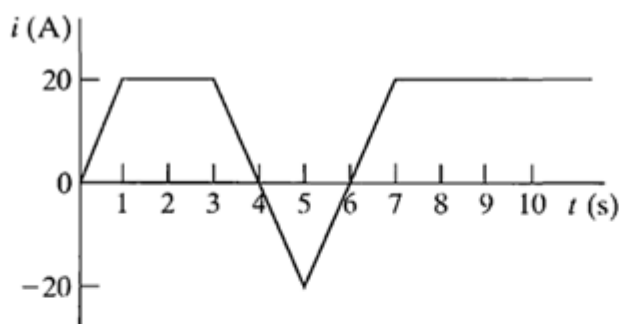
- a) Sketch the power versus time plot for $0 < t < 10$ s.
b) Calculate the energy delivered to the circuit element at $t = 1$, 6, and 10 s.



(a)

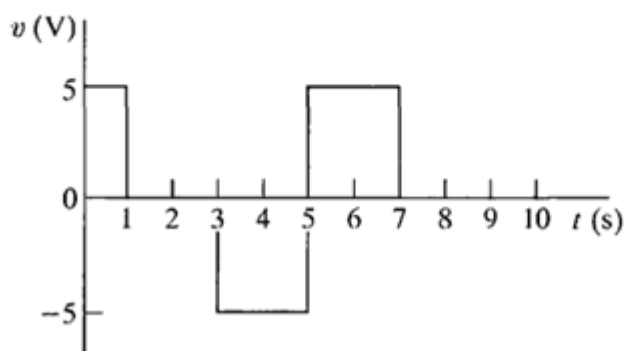


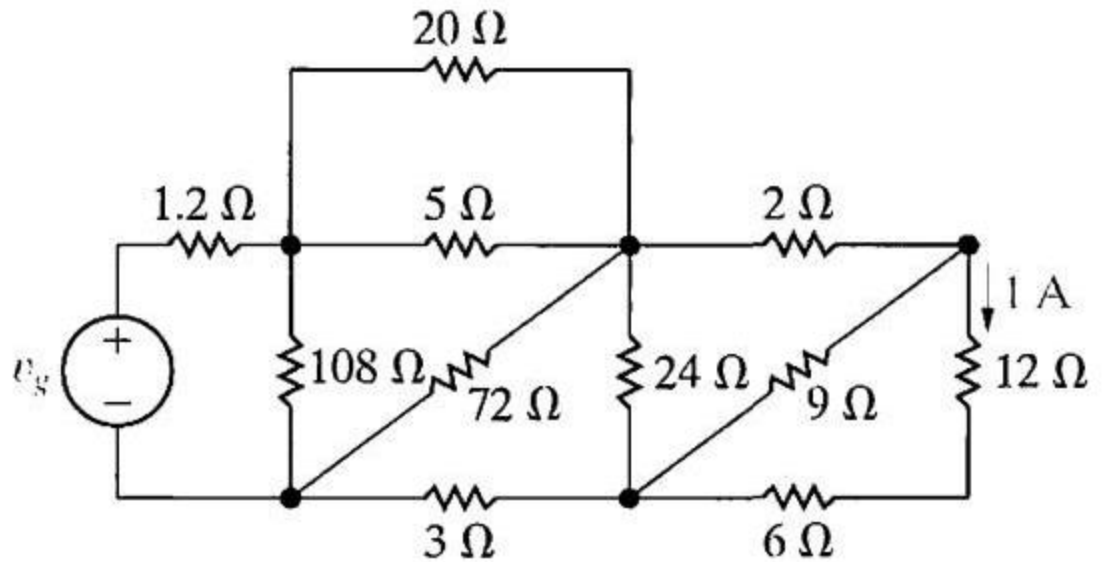2. The current in the 12 ohm resistor in the circuit in Fig. below is 1 A, as shown.
- a) Find v_g . [5]
b) Find the power dissipated in the 20 ohm resistor. [5]




3. Find R for the circuit in Figure below


[5]

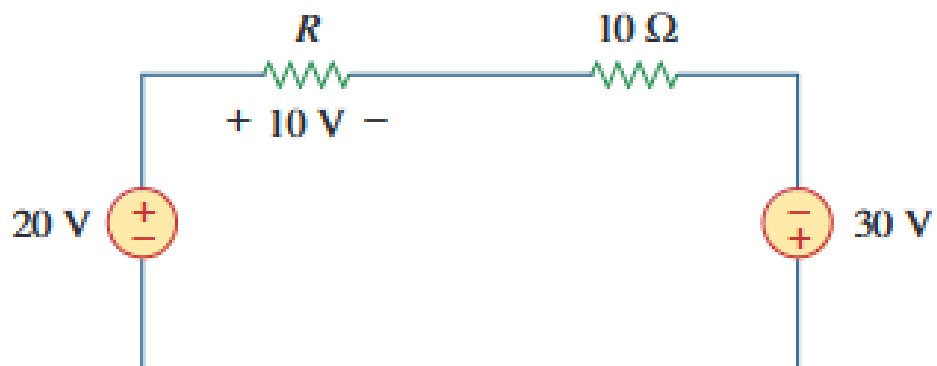

4. Find equivalent resistance between a-b terminal

[10]

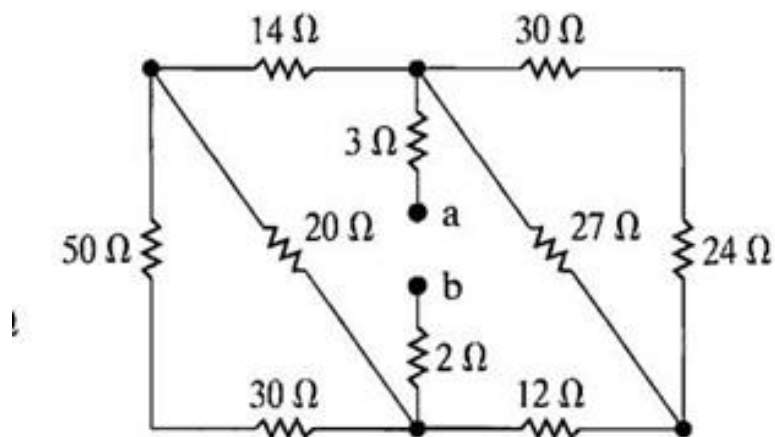

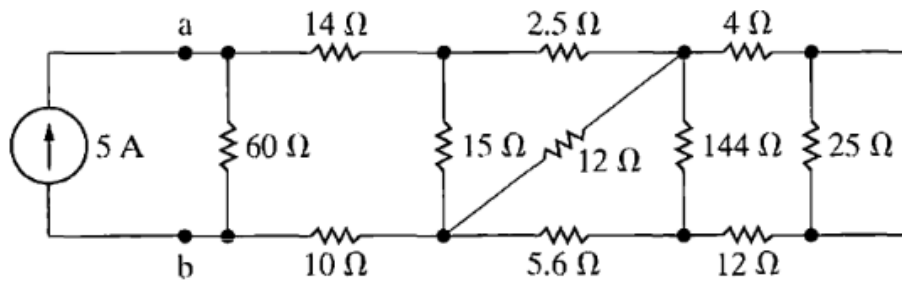

5. Use nodal analysis to find v_1, v_2, v_3 and i_o [15]

