

**UNITED INTERNATIONAL UNIVERSITY (UIU)**  
Dept. of Computer Science & Engineering  
Course No: EEE 2113    Title: Electrical Circuits (Summer 2024)  
Assignment - 01

1. Determine the followings for the circuit shown in Figure 1. (10)
  - a. Determine the total impedance of the circuit. (3)
  - b. Determine  $i(t)$  where  $i(t)$  is the total current of the circuit. (2)
  - c. Determine the voltage( $v_o$ ) across the  $0.1\text{H}$  inductor. (3)
  - d. Determine the phase difference between the source voltage and the voltage across the  $0.1\text{H}$  inductor and also determine which one is leading. (2)

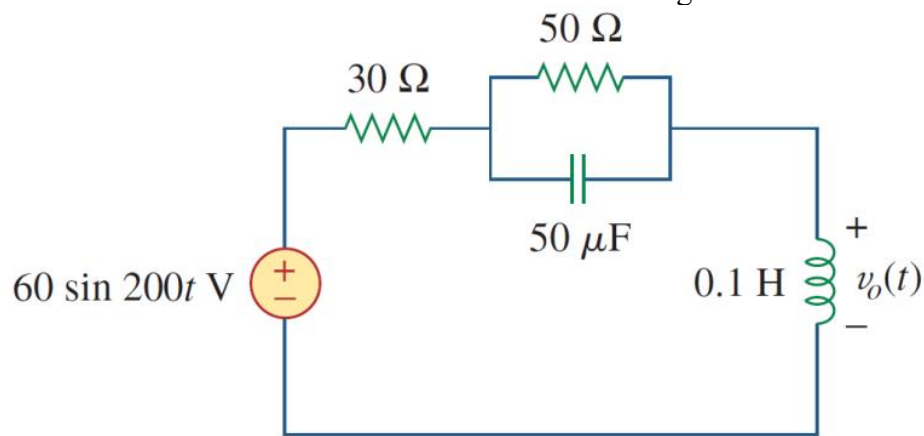


Figure 01

2. For the circuit in Figure 2, find the Thevenin equivalent circuits at terminals a-b. (10)

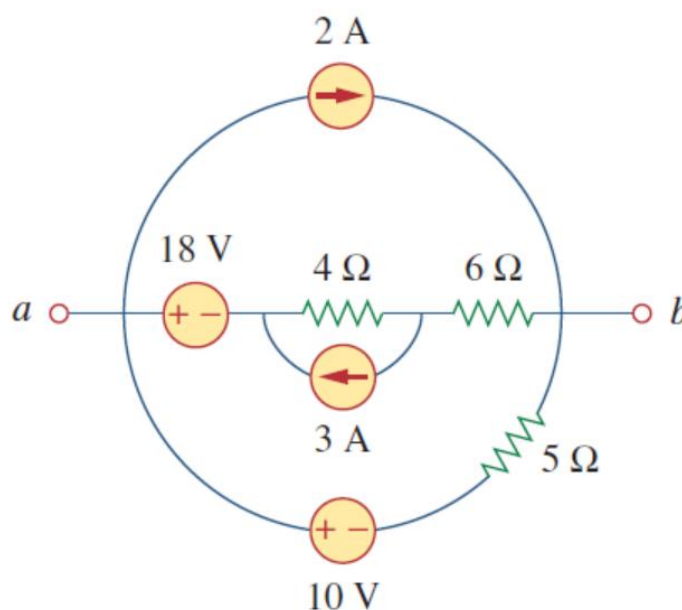


Figure 02

2. Use the Superposition Principle to solve for  $I_1$ ,  $I_2$ ,  $I_3$  in the following circuit

