



United International University (UIU)
Dept. of Computer Science & Engineering (CSE)
MID Exam, Trimester: Spring 2024

Course Code: CSE 113/EEE 2113; Course Title: Electrical Circuits

Total Marks: 30; Duration: 1 hour 30 min

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

Question 1: Answer all the questions.

(8 Marks)

Answer the following questions for the circuit shown in **Figure 1**:

[4+4]

- The current shown in **Figure 1** is flowing through a 5Ω wire. Now, draw the charge, q vs. time graph for this current considering the initial charge in the wire is $1C$ at $t=0s$.
- Draw the power absorbed by this wire vs. time graph.

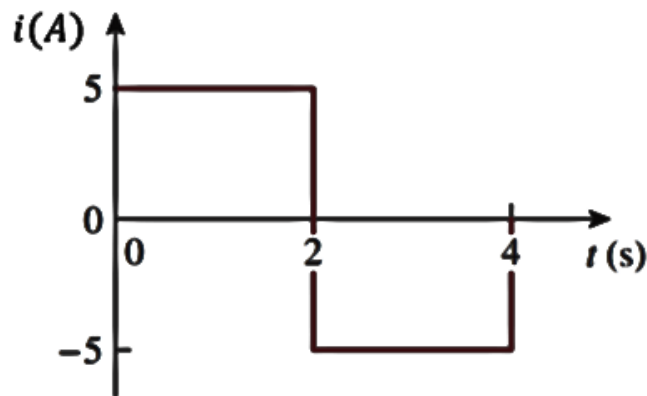


Figure 1

Question 2: Answer all the questions.

(6 Marks)

For the circuit shown in **Figure 2**, answer the following questions:

[3+3]

- Write the KVL equations for the Loops, $L1$ and $L2$.
- Calculate the values of V_x and I_y .

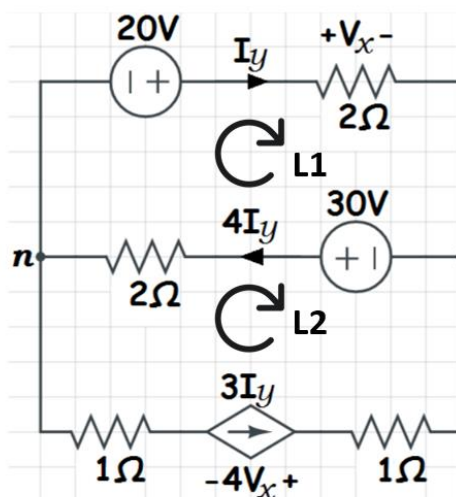
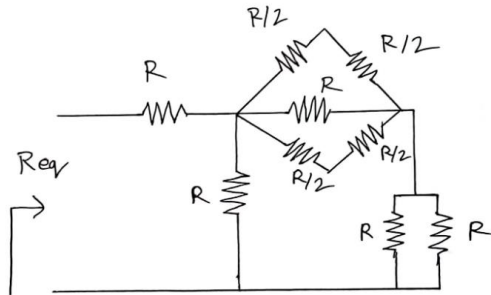
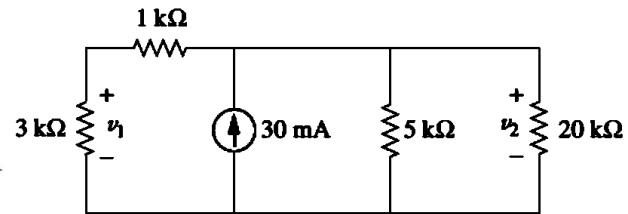


Figure 2.

Question 3: Answer all the questions**(8 Marks)**Answer the following questions for the circuit shown in **Figure 3 (a-b)**:



[4+4]

- If $R_{eq} = 10\ \Omega$ for the circuit shown in **Figure 3(a)**, then find the value of R .
- Figure out the values of v_1 , v_2 in the circuit shown in **Figure 3(b)**.

**Figure 3a****Figure 3b****Question 4: Answer all the questions.****(8 Marks)**Answer the following questions for the circuit shown in **Figure 4 (a-b)**:

[4+4]

- Find the current, i , and the voltage, V_o in **Figure 4a** using mesh analysis.
- Using nodal analysis in **Figure 4b**, find the values of v_1 and v_2 .

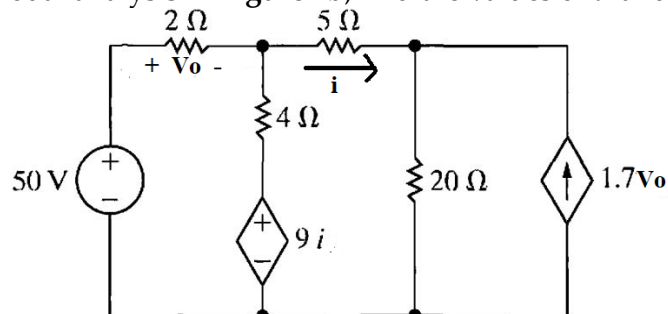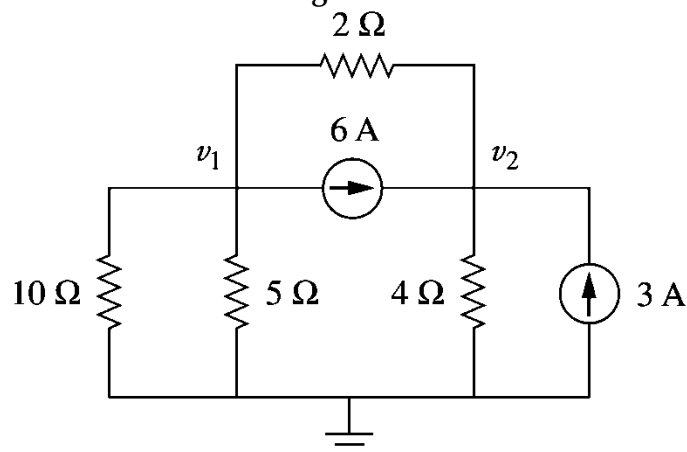**Figure 4a.****Figure 4b.**