

Question 1: Answer all the questions.

(10 Marks)

For the above circuit shown in **Figure 1**, determine I_o using Superposition and the power dissipated in 15Ω resistance.


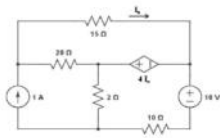


Figure 1.

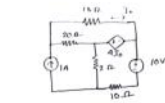

$$I_o = I_{o1} + I_{o2}$$

$$\text{where, } I_{o1} \rightarrow 3A$$

$$I_{o2} \rightarrow 10V$$

For I_{o1} ,



$$\text{For mesh-1, } i_1 = 1A$$

$$\text{For mesh-2, } 2(i_1 - i_2) + 4I_o + 10i_2 = 0$$

$$\Rightarrow -2i_1 + 12i_2 + 4i_2 = 0 \quad \therefore [i_1 = 1A]$$

$$\Rightarrow -2 \times 1 + 12i_2 + 4i_2 = 0$$

$$\Rightarrow 12i_2 + 4i_2 = 2 \quad \therefore \text{--- (1)}$$

For mesh-3,

$$15i_3 - 4I_o + 20(i_3 - i_1) = 0$$


$$\Rightarrow 15i_3 - 4i_3 + 20i_3 - 20i_1 = 0$$

$$\Rightarrow 31i_3 - 20 \times 1 = 0$$

$$\Rightarrow i_3 = \frac{20}{31} = 0.6452A$$

$$\therefore I_{o1} = i_3 = 0.6452A$$

For I_{o2} ,

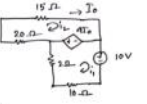

For mesh-1,

$$10i_1 + 2i_1 + 4I_o + 10 = 0$$

$$\Rightarrow 12i_1 + 4i_2 = -10 \quad \therefore [I_o = I_1 = i_2]$$

For mesh-2,

$$15i_2 - 4I_o + 20i_2 = 0$$

$$\Rightarrow 35i_2 - 4i_2 = 0$$

$$\Rightarrow 31i_2 = 0$$

$$\therefore i_2 = 0$$

$$\therefore I_{o2} = i_2 = 0A$$

$$\therefore I_o = I_{o1} + I_{o2} = 0.6452 + 0 = 0.6452A$$

power dissipated; $P = I_o^2 R$
 $= (0.6452)^2 \times 15$
 $= \boxed{6.34} \text{ W}$ Ans. *calculated by own.*

Question 2: Answer all the questions.

(10 Marks)

For the circuit shown in **Figure 2**, determine the following questions:

- i) For the circuit shown below, find the thevenin equivalent circuit at the **A-B** terminal. [5+2]
 ii) For any resistance connected right to **A-B** terminal, what will be the maximum power delivered to the resistance?
 iii) If 10Ω resistance is connected between **A-B**, then would maximum power be achieved? If not then what should you do?

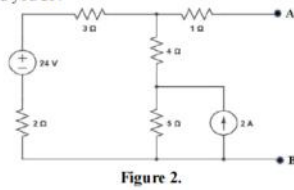


Figure 2.

ii) Max power


$$P_{max} = \frac{V_{TH}^2}{4 R_{TH}} = \frac{19^2}{4 \times 9.219} = 21.417 \text{ W}$$

iii) P_{max} will not occur if


$$R_L = 10 \Omega$$

As we know for P_{max} ,

$$R_L = R_{TH} = 9.219 \Omega$$

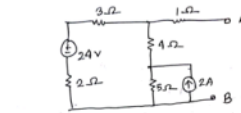


For R_{TH} ,

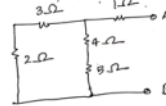

$$R_{TH} = 1 + ((2+2) \parallel (4+5)) = 9.219 \Omega$$

For V_{TH} ,

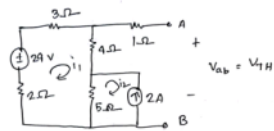

From mesh-2,

$$i_2 = -2 \text{ A}$$

For mesh-1,

$$3i_1 + 4i_1 + 5(i_1 - i_2) + 2i_1 - 24 = 0$$

$$\Rightarrow 14i_1 - 5i_2 - 24 = 0$$

$$\Rightarrow 14i_1 = 24 + 5(-2)$$

$$\therefore i_1 = 1 \text{ A}$$

$$V_{TH} = 4i_1 + 5(i_1 - i_2) = 4 \times 1 + 5(1 - (-2)) = 19 \text{ V}$$

Question 3: Answer all the questions

(10 Marks)

For the circuit shown in Figure 1, $V_s(t) = 15 \cos(100t + 30^\circ)$ V. Now, determine the following quantities:
 (a) Find equivalent impedance at terminals a-b.
 (b) Find I_1 , V_{ab} , V_{bc} and V_{ca} .

Page 1 of 2

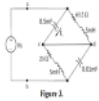


Figure 1

Let,

Z_1 = Impedance of the 5 mH inductor

Z_2 = Impedance of the 63.2 Ω resistance
 in series with the 63.2 Ω resistance

Z_3 = Impedance of the 5 mH inductor
 in series with the 20 Ω resistance

Z_4 = Impedance of the 0.01 μF capacitor

Here, $V_s(t) = 15 \cos(100t + 30^\circ)$ V, $\omega = 100$


$$Z_1 = \frac{1}{j\omega L} = \frac{1}{j \times 100 \times 5 \times 10^{-3}} = -20j$$

$$Z_2 = 63.2 + j\omega L = 63.2 + j \times 100 \times 5 \times 10^{-3} = 63.2 + 0.5j$$

$$Z_3 = 20 + j\omega L = 20 + j \times 100 \times 5 \times 10^{-3} = 20 + 0.5j$$

$$Z_4 = \frac{1}{j\omega C} = \frac{1}{j \times 100 \times 0.01 \times 10^{-6}} = -1000j$$

So,

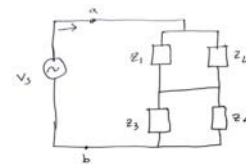


$$(a) Z_{ab} = (Z_1 \parallel Z_2) + (Z_3 \parallel Z_4) = 25.196 - 21.617j = 33.199 \angle -40.629^\circ$$

$$(b) I = \frac{V}{Z_{ab}} = \frac{15 \angle 30^\circ}{33.199 \angle -40.629^\circ} = 0.4518 \angle 70.629^\circ$$

$$I_1 = \frac{Z_2}{Z_1 + Z_2} \times I = 0.4318 \angle 88.229^\circ$$

$$\therefore I_1(t) = 0.4318 \cos(100t + 88.229^\circ)$$
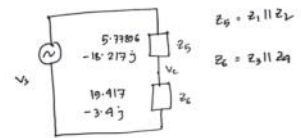
$$V_{ca}(t) = 0 \text{ because } V_c(t) = V_a(t)$$



$$V_c = \frac{Z_c}{Z_5 + Z_6} \times V_s = 15.472 \angle 92.466^\circ$$

$$\therefore V_c(t) = V_a(t) = 15.472 \cos(100t + 92.466^\circ)$$

Question 4: Answer all the questions.

(10 Marks)

For the waveform shown in **Figure 4a**, determine the rms value of the current, i_{rms} . Also, determine the power absorbed by 5Ω resistance for the circuit shown in **Figure 4b**.

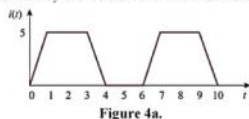


Figure 4a.

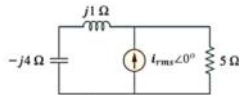



Figure 4b.

$$I_{rms}^2 = \frac{1}{T} \int_0^T i^2(t) dt = \frac{1}{6} \left[\int_0^1 25t^2 dt + \int_1^3 25 dt + \int_3^4 (-5t+20)^2 dt \right]$$

$$I_{rms}^2 = \frac{1}{6} \left[25 \frac{t^3}{3} \Big|_0^1 + 25(3-1) + \left(25 \frac{t^3}{3} - 100t^2 + 400t \right) \Big|_3^4 \right] = 11.1056$$

$$I_{rms} = 3.332 \text{ A}$$

$$I_{rms} = 3.332 \text{ A}$$

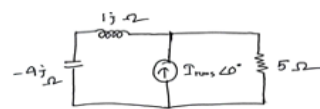

↓



As, $1j$ inductor and $-4j$ capacitor are in series
So, $Z_1 = 1j - 4j$
 $= -3j$

$$i_2 = \frac{Z_1}{Z_1 + Z_2} \times I$$

$$= \frac{-3j}{-3j + 5} \times 3.332 \angle 0^\circ$$

$$\therefore i_2 = 1.7143 \angle -59.036^\circ$$

$$P_{5\Omega} = \frac{1}{2} I_{rms}^2 R = \frac{1}{2} \times (1.7143)^2 \times 5 = 7.397 \text{ watt}$$

Scanned with CamScanner